

## ELE613 – SWITCH MODE POWER SUPPLIES HOMEWORK 1

**Q1)** The topology to be analyzed and simulated in this homework is a buck converter with the following specifications:

- $V_d = 8\text{ Vdc}$
- $L = 10\mu\text{H}, r_L = 10\text{m}\Omega$
- $C = 100\mu\text{F}$
- $R_{load} = 0.5\ \Omega$
- $f_s = 50\text{ kHz}$
- $D = 0.75$

For simulations, Simulink environment is preferred and the simulation model is shown in Figure 1, below.

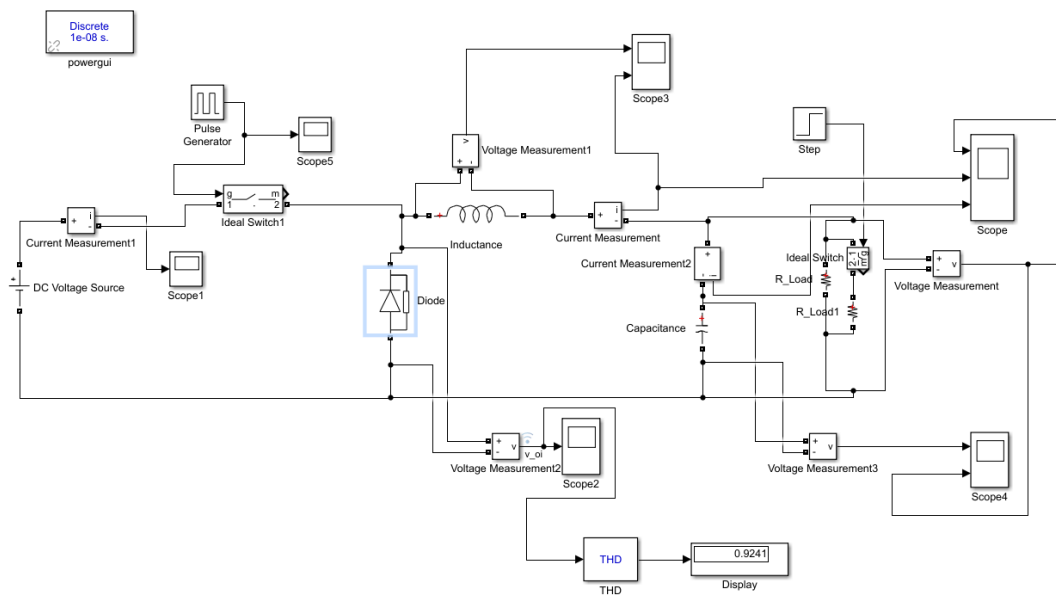


Figure 1: Simulation Model of the Buck Converter

Inductor voltage and current waveforms (for part (a)) and output voltage, inductor current and capacitor current waveforms (for part (b)) are provided in Figures 2 and 3, respectively.

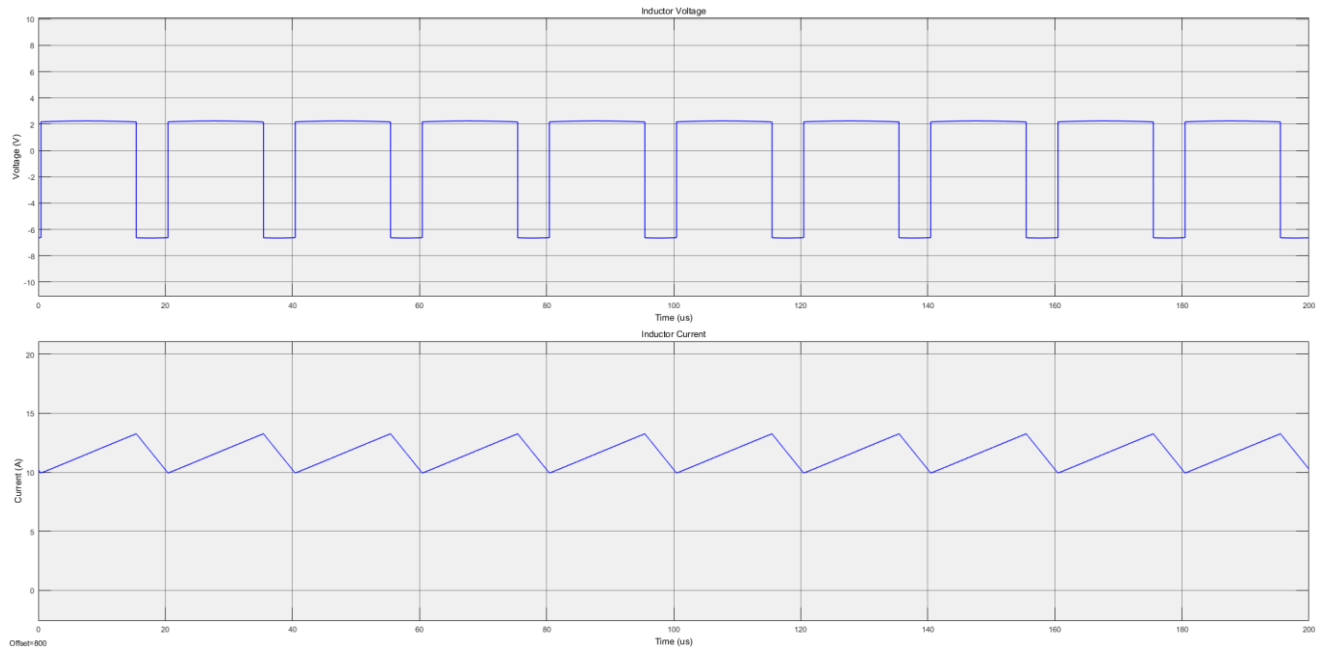


Figure 2: Inductor Voltage and Current

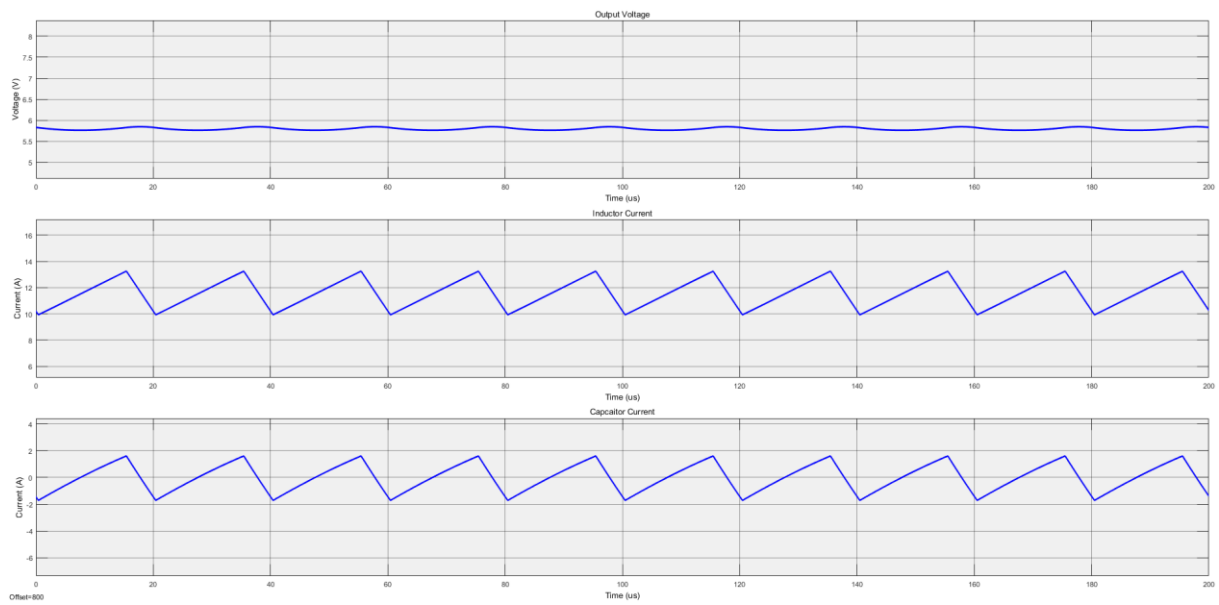


Figure 3: Output Voltage, Inductor Current and Capacitor Current

**Q2)** FFT analysis is performed using powergui toolbox of Simulink. Harmonic components are shown with respect to their orders, on the graph given in Figure 4, below.

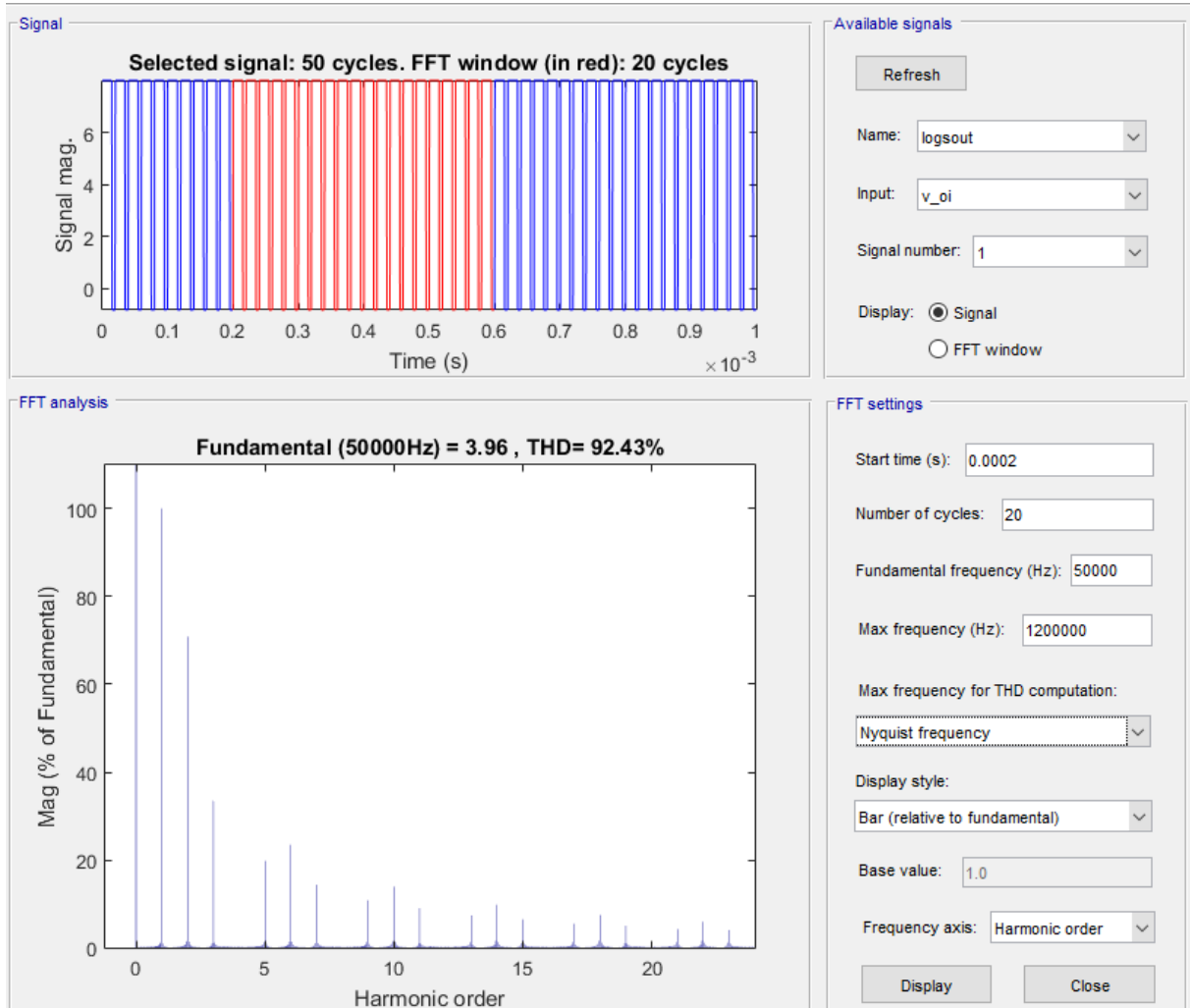


Figure 4: FFT Analysis Results

**Q3)** Discontinuous mode inductor voltage and current waveforms and output voltage waveform are given in Figure 5 and 6, respectively.

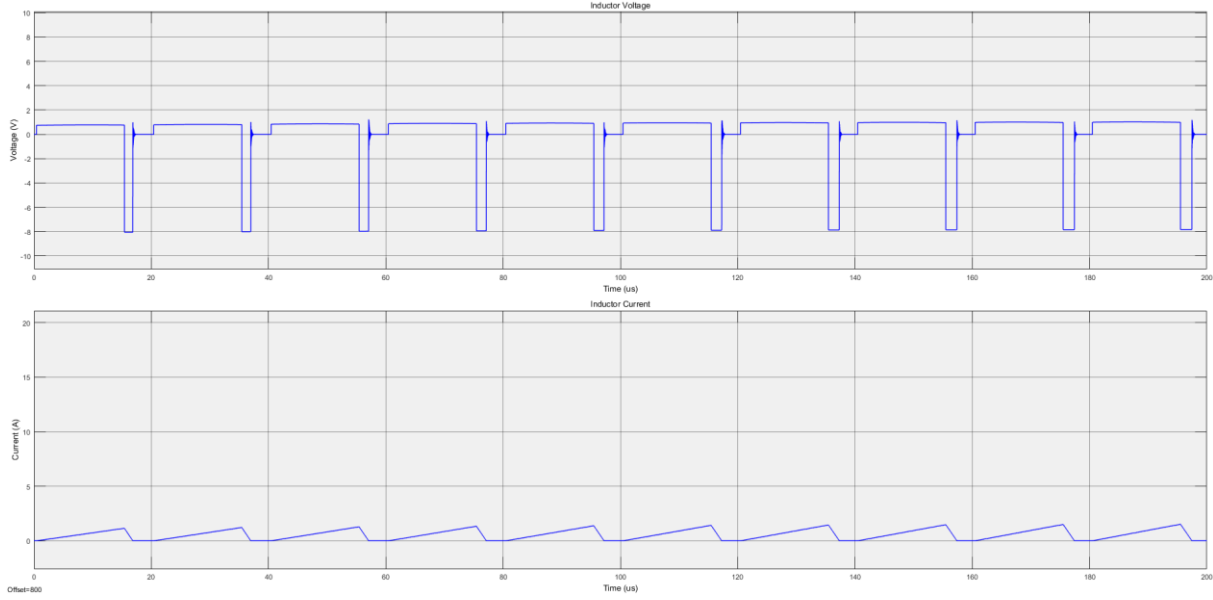


Figure 5: Discontinuous Mode Inductor Voltage and Current

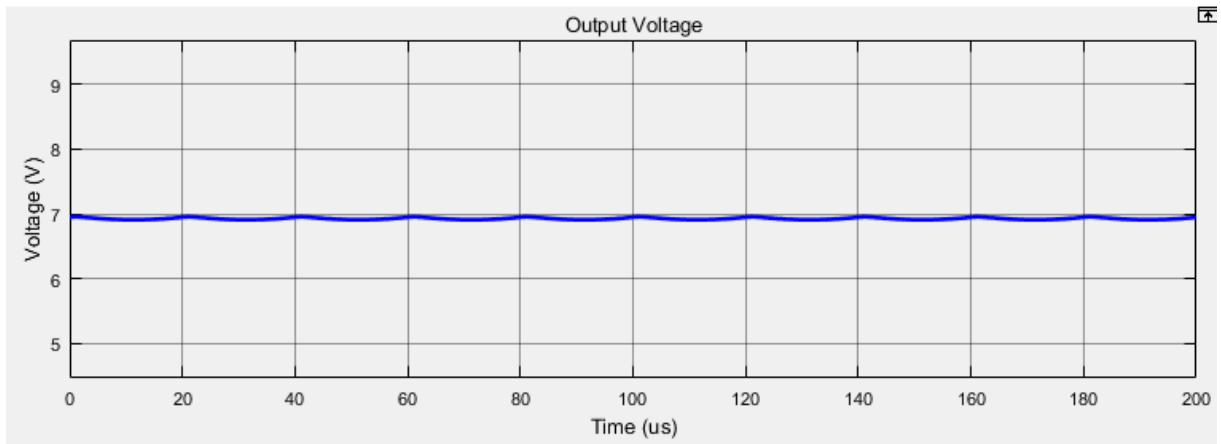


Figure 6: Discontinuous Mode Output Voltage Waveform

Simulation results should agree with the following equation:

$$\frac{V_o}{V_d} = \frac{D^2}{D^2 + \frac{1}{4} \left( \frac{I_o}{\frac{V_d}{8Lf_s}} \right)}$$

Replacing the variables as follows:

$$f_s = 50 \text{ kHz}$$

$$D = 0.75$$

$$I_o = \frac{V_o}{10}$$

$$L = 10 \mu\text{H}$$

$$V_d = 8\text{V}$$

We get the following equality:

$$\frac{V_o}{8} = \frac{\frac{9}{16}}{\frac{9}{16} + \frac{1}{4} \left( \frac{V_o}{10} * 50 * 10^3 * 10 * 10^{-6} \right)}$$

$$\frac{V_o}{8} = \frac{9}{9 + \frac{V_o}{5}}$$

$$V_o = 6.93 \text{ V}$$

This result is verified with the output voltage waveform of simulation, given in Figure 6.

**Q4)** Analytical calculation can be done as follows:

$$\Delta v_c = \frac{\Delta i_L}{8f_s C} = \frac{\Delta i_L}{40}$$

In Figures 7, 8 and 9, capacitor voltage and inductor current ripple waveforms and their peak to peak values are given, respectively.

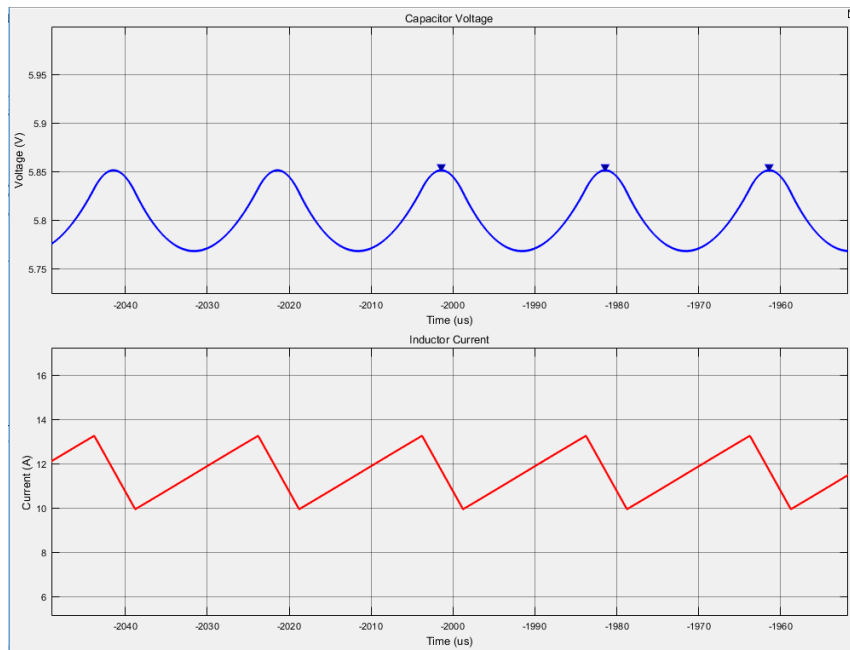


Figure 7: Capacitor Voltage and Inductor Current

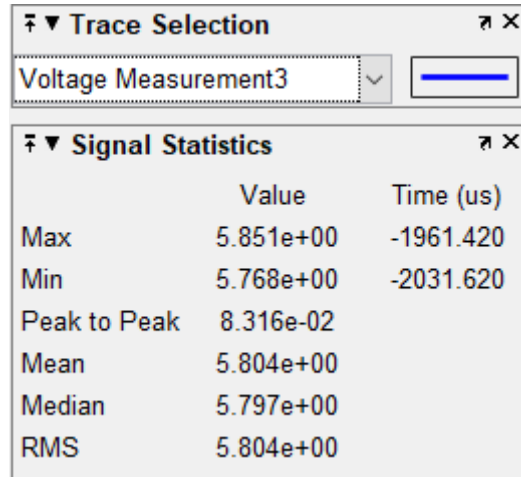


Figure 8: Capacitor Voltage Peak-To-Peak Value

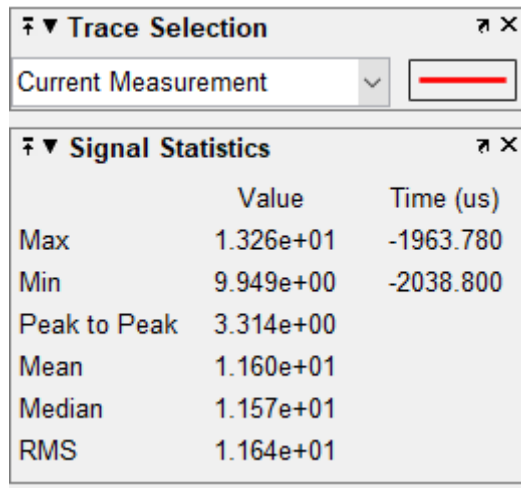


Figure 9: Inductor Current Peak-To-Peak Value

As provided in figures, capacitor voltage ripple is 40 times larger than the inductor current ripple, which actually agrees with the analytical calculations.

**Q5)** Capacitor current swing is equal to inductor current swing and average of the capacitor current is zero, therefore it can be calculated as the RMS of a triangular wave with amplitude  $\frac{\Delta i_L}{2}$ .

$$I_{C,rms} = \frac{\Delta i_L}{2\sqrt{3}} = \frac{V_o(1-D)}{2\sqrt{3}Lf_s} = I_o * R_{load} * \frac{0.25}{2\sqrt{3} * 0.5} = 0.072I_o$$

**Q6)** In the presence of ESR, we may assume that output voltage ripple is caused only by voltage drop on ESR. Therefore it can be calculated as:

$$\Delta v = \Delta i_c * r_{ESR}$$

Here, we know that current ripple on the capacitor is equal to that of the inductance, hence:

$$\Delta v = \Delta i_L * r_{ESR} = \frac{V_o(1-D)}{Lf_s} * r_{ESR} = 4 * 0.1 = 0.4 \text{ V}$$

Simulation results for this part are given in Figures 10, 11 and 12.

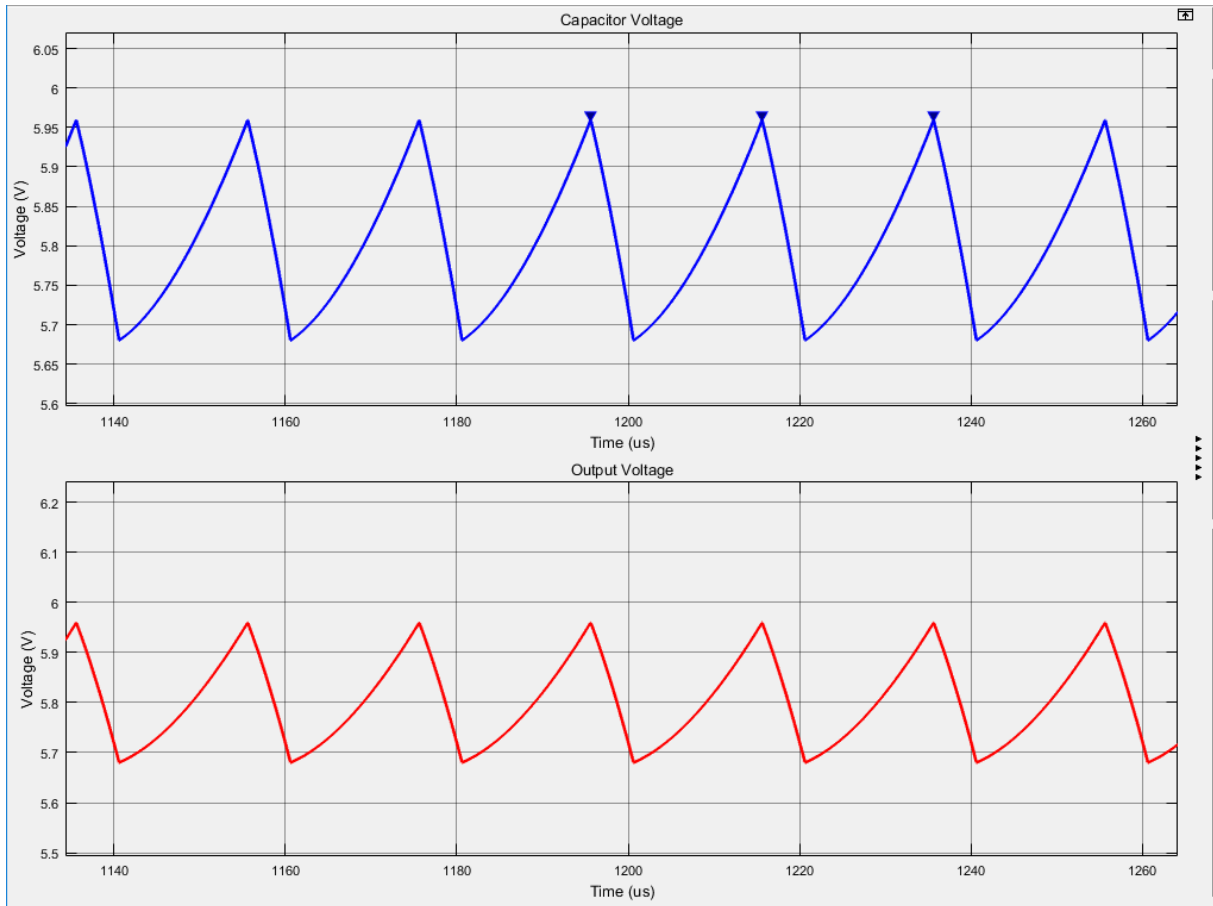


Figure 10: Capacitor and Output Voltage Waveforms

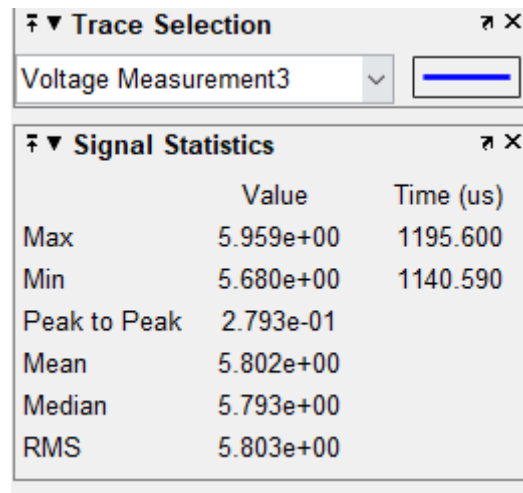


Figure 11: Capacitor Voltage Ripple

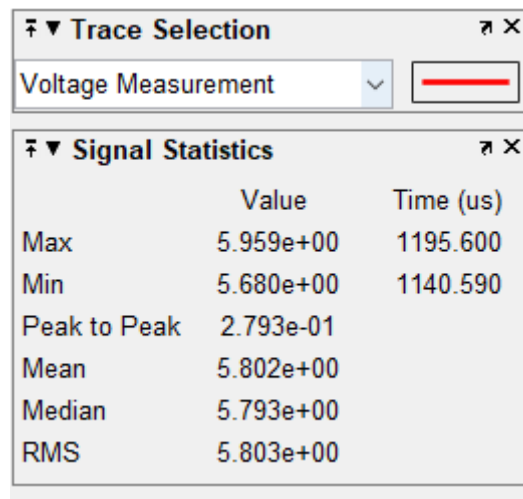


Figure 12: Output Voltage Ripple

As can be observed in simulation results, capacitor (including ESR) voltage ripple is equal to output voltage ripple, which verifies the initial assumption.